

## Practica No. 5 Diseño de un Multiplicador

**Objetivo:** Diseñar un módulo de multiplicación utilizando diferentes métodos, entender las ventajas y desventajas de cada uno de ellos. Aprender a usar procesos y funciones en VHDL.

**Desarrollo:** Para cada uno de los siguientes apartados, realizar los diseños electrónicos que se piden.


**Duración:** 1 semana.

1.- La forma más directa de hacer la multiplicación es a través de una tabla en donde la concatenación del multiplicando y del multiplicador forman la dirección de una localidad de memoria en donde se encuentra el resultado. Instrumente la descripción de este Hardware utilizando el lenguaje VHDL para la multiplicación de dos números de 4 bits con el resultado de 8 bits. Pruebe su tabla en el sistema de desarrollo de Quartus, incluya un módulo de prueba en donde se carguen los valores iniciales del multiplicando y multiplicador, muestre el resultado en los 8 leds de la tarjeta. Utilice este módulo de prueba para los siguientes incisos.

2.- Se puede hacer también la multiplicación utilizando un algoritmo que realiza sumas y corrimientos como se muestra en el apéndice A en código VHDL. Explique el algoritmo y los módulos que se presentan en este apéndice, pruebe este algoritmo también en el sistema de desarrollo de Quartus.

3.- Otra forma de hacer la multiplicación es a través de compuertas ANDs, concatenación de ceros y un sumador como se muestra en el siguiente ejemplo:

	A	0	0	0	0	1	1	1	
<b>X</b>	<b>B</b>	0	0	0	0	1	1	0	1
		0	0	0	0	1	1	1	“0”
		0	0	0	0	0	0	0	“0”
		0	0	0	1	1	1	“0”	“0”
		0	0	1	1	1	“0”	0	0”
	<b>Y</b>	0	1	0	1	1	0	1	1

 

\* Se agradece el apoyo otorgado para el desarrollo de esta practica a DGAPA-UNAM PAPIME PE102213

En el apéndice B se muestra este diseño en VHDL usando librerías propias que sustituyen la función AND estándar, implemente estas funciones en el sistema de desarrollo Quartus.

4.- Utilice el módulo de multiplicación incluido en las librerías de Quartus.

Compare los tres diseños anteriores con éste módulo, indicando las ventajas y desventajas para diferentes tamaños en el número de bits de los operandos: 4, 8, y 16 y 32 bits.

---

## APENDICE A

### Multiplicación usando algoritmos

---

-----  
-- state\_machine\_multiplier.vhd  
-----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity state_machine_multipli is
    Port ( clk : in  STD_LOGIC;

          START: in STD_LOGIC;
          DONE  : out STD_LOGIC;
          A, B  : In  unsigned (3 downto 0);
          Y    : Out unsigned (7 downto 0);
          reset : in  STD_LOGIC;
          out_epresente :out std_logic_vector (1 downto 0));

end state_machine_multipli;

architecture Behavioral of state_machine_multipli is

    constant size_product: integer range 0 to 256 :=8;
    constant num_cnt: unsigned (3 downto 0) := X"3";
    signal esiguiente : std_logic_vector (1 downto 0) := B"00";
    signal load: STD_LOGIC;
    signal load_cnt: STD_LOGIC;
    signal inc_cnt: STD_LOGIC;
    signal load_product: STD_LOGIC;
    signal flg_cnt: STD_LOGIC := '0';
    signal reset_product: STD_LOGIC;
    signal multiplier: unsigned (3 downto 0);
    signal multiplicand: unsigned (3 downto 0);
    shared variable product: unsigned (size_product downto 0);
    shared variable partial_sum: unsigned (4 downto 0);
    shared variable prev_carry: STD_LOGIC;
    shared variable counter: unsigned (3 downto 0);
    signal shift_right_P: STD_LOGIC;
    signal shift_right_M: STD_LOGIC;
    signal add_product: STD_LOGIC;

    constant s0 : std_logic_vector(1 downto 0) := "00";
    constant s1 : std_logic_vector(1 downto 0) := "01";
    constant s2 : std_logic_vector(1 downto 0) := "10";
    constant s3 : std_logic_vector(1 downto 0) := "11";
    constant ZERO : unsigned (3 downto 0) := "0000" ;

    constant ZERO_8: unsigned (7 downto 0) := "00000000" ;
```

```
begin
```

```
state_machine: process (clk,reset,esiguiente, START)
```

```
begin
```

```
    if reset='0' then
        siguiente <=s0;
        reset_product <= '1';
    elsif rising_edge (clk) then
        case siguiente is
            when s0 =>
                DONE <= '0';
                inc_cnt <= '0';
                load_product <= '0';
                shift_right_M <= '0';
                shift_right_P <= '0';

                if START='0' then
                    siguiente<= s0;
                    load <= '0';
                    load_cnt <= '0';
                    reset_product <= '0';
                    load_product <= '0';
                else
                    siguiente<= s1;
                    load <= '1';
                    load_cnt <= '1';
                    reset_product <= '1';
                    load_product <= '0';
                end if;
            end if;
```

```
            when s1 =>
```

```
                DONE <= '0';
                inc_cnt <= '1';
                load_product <= '1';
                load <= '0';
                load_cnt <= '0';
                siguiente<= s2;
                shift_right_M <= '1';
                shift_right_P <= '0';
                reset_product <= '0';
```

```
            when s2 =>
```

```
                DONE <= '0';
                inc_cnt <= '0';
                load_product <= '0';
```

```

        load <= '0';
        load_cnt <= '0';
        shift_right_M <= '0';
        shift_right_P <= '1';
        reset_product <= '0';

        if flg_cnt = '0' then
            esiguiente <= s1;
        else
            esiguiente <= s3;
        end if;

    when s3 =>

        DONE <= '1';
        inc_cnt <= '0';
        load_product <= '0';
        load <= '0';
        load_cnt <= '0';
        esiguiente <= s0;
        shift_right_M <= '0';
        shift_right_P <= '0';
        reset_product <= '0';
        add_product <= '0';

    when others => null;

end case;

out_epresente <= esiguiente;
Y <= product(7 downto 0);

end if;

end process state_machine;

multplr: process (clk,load,shift_right_M,A)

begin

    if rising_edge (clk) then
        if load = '1' then
            multiplier <= A;
        elsif shift_right_M = '1' then
            multiplier <= ('0' & multiplier(3 downto 1));
        end if;
    end if;

end process multplr;

multpl: process (clk,load,B)

```

```

begin
    if rising_edge (clk) then
        if load ='1' then
            multiplicand <= B;
        end if;
    end if;
end process multipl;

```

```

counter_module: process (clk,load_cnt)

```

```

begin
    if rising_edge (clk) then
        if load_cnt ='1' then
            counter := num_cnt;
            flg_cnt <= '0';

            elsif inc_cnt ='1' then
                counter := counter - 1;
            end if;

            if counter = ZERO then
                flg_cnt <= '1';
            end if;
        end if;
    end if;

```

```

end process counter_module;

```

```

and_sum: process (clk,multiplier,multiplicand)

```

```

begin
    if reset_product = '1' then
        partial_sum := "00000";
        prev_carry := '0';
    end if;

    if load_product = '1' then
        if multiplier(0) ='1' then
            partial_sum := product(8 downto 4) + ('0' & multiplicand);
        else
            partial_sum := ('0' & product(7 downto 4));
        end if;
    end if;

```

```

end process and_sum;

```

```

prod: process (clk,reset_product,load_product,shift_right_P)

```

```
begin
  if rising_edge (clk) then
    if reset_product = '1' then
      product := "00000000";
    end if;

    if load_product = '1' then
      product(8 downto 4) := partial_sum;
    elsif shift_right_P = '1' then
      product := '0' & product(8 downto 1);
    end if;
  end if;
end process prod;

end Behavioral;
```

---

**APENDICE B**  
**Multiplicación usando ANDs, sumador y concatenación de ceros**

---

-----  
-- my\_multiplier.vhd -  
-----

```
library my_library;  
use my_library.ARITH_types.ALL;
```

```
entity my_multiplier is  
  Port ( START: in STD_LOGIC;  
        DONE : out STD_LOGIC;  
        A, B : In unsigned (3 downto 0);  
        Y   : Out unsigned (7 downto 0));  
end my_multiplier;
```

```
architecture Behavioral of my_multiplier is
```

```
  constant ZERO : unsigned (3 downto 0) := "0000" ;
```

```
  Begin
```

```
  process (START,A,B)
```

```
  begin
```

```
    if START='0' then DONE <= '0';
```

```
    else
```

```
      Y <= (B(0) and (ZERO(3 downto 0) & A)) +  
          (B(1) and (ZERO(3 downto 1) & A & ZERO(0 downto 0))) +  
          (B(2) and (ZERO(3 downto 2) & A & ZERO(1 downto 0))) +  
          (B(3) and (ZERO(3 downto 3) & A & ZERO(2 downto 0))) ;
```

```
      DONE <= '1';
```

```
    end if;
```

```
  end process;
```

```
end Behavioral;
```

-----  
-- my\_library.vhd -  
-----

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
package ARITH_types is
```

```
  function "and" (L: std_ulogic ; R: unsigned) return unsigned;
```

```
end ARITH_types;
```



```
package body ARITH_types is
```

```
function "and" (  
  L: std_ulogic ;  
  R: unsigned  
) return unsigned is
```

```
begin  
  case L is  
    when '0' | 'L' =>  
      return (R'range => '0');  
    when '1' | 'H' =>  
      return R ;  
    when others =>  
      return (R'range => 'X');  
  end case;  
end "and";
```

```
end ARITH_types;
```